

EE160 Lab Assignment-3

Lab section 1A

Power Measurement in 3-Phase Electric Circuit

Karan Acharya

202251064

Objectives:

On Simulink, design a circuit with Y-connected 3-phase AC sources (220V, 50 Hz) and Y-connected 3-phase RLC branch.

Parameters:

Input voltage = 220V

Frequency = 50Hz


Phase of A = 0

Phase of B = -120


Phase of C = -240

$R=1\ \Omega$ $L=10^{-3}\text{ H}$ $C=10^{-6}\text{ F}$

Circuit :

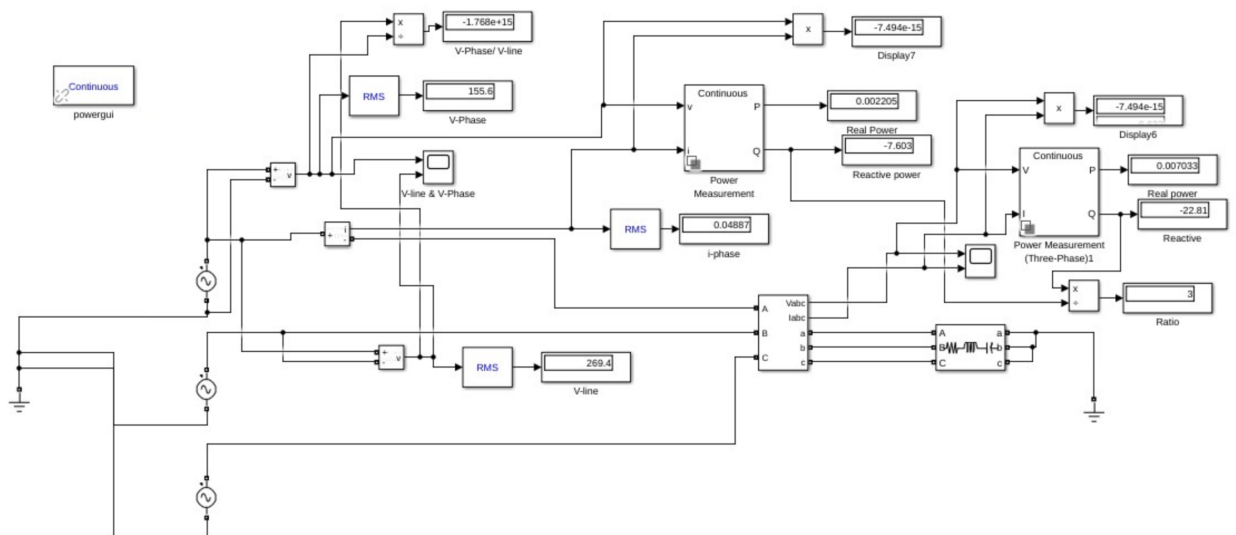

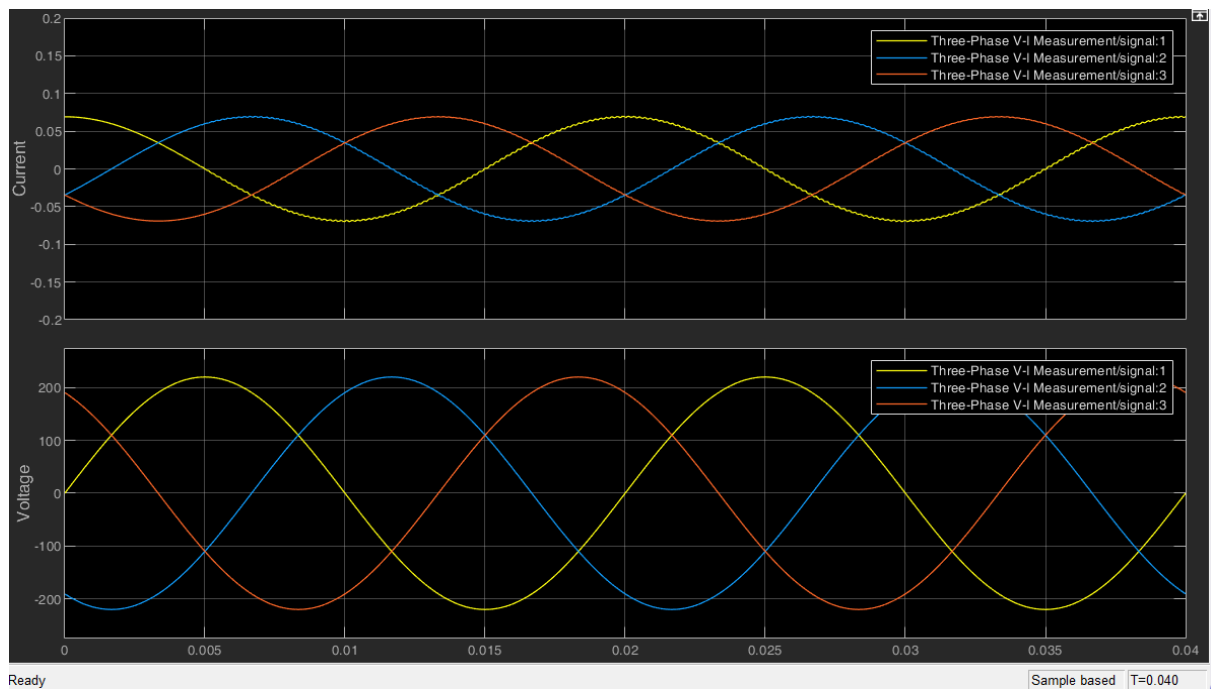
Scope 1 : Three Phase Current And Voltage



Result:

At any point the sum of current of phase A, B and C is equal to Zero.


Scope 2 : Total Power (Reactive + Real)

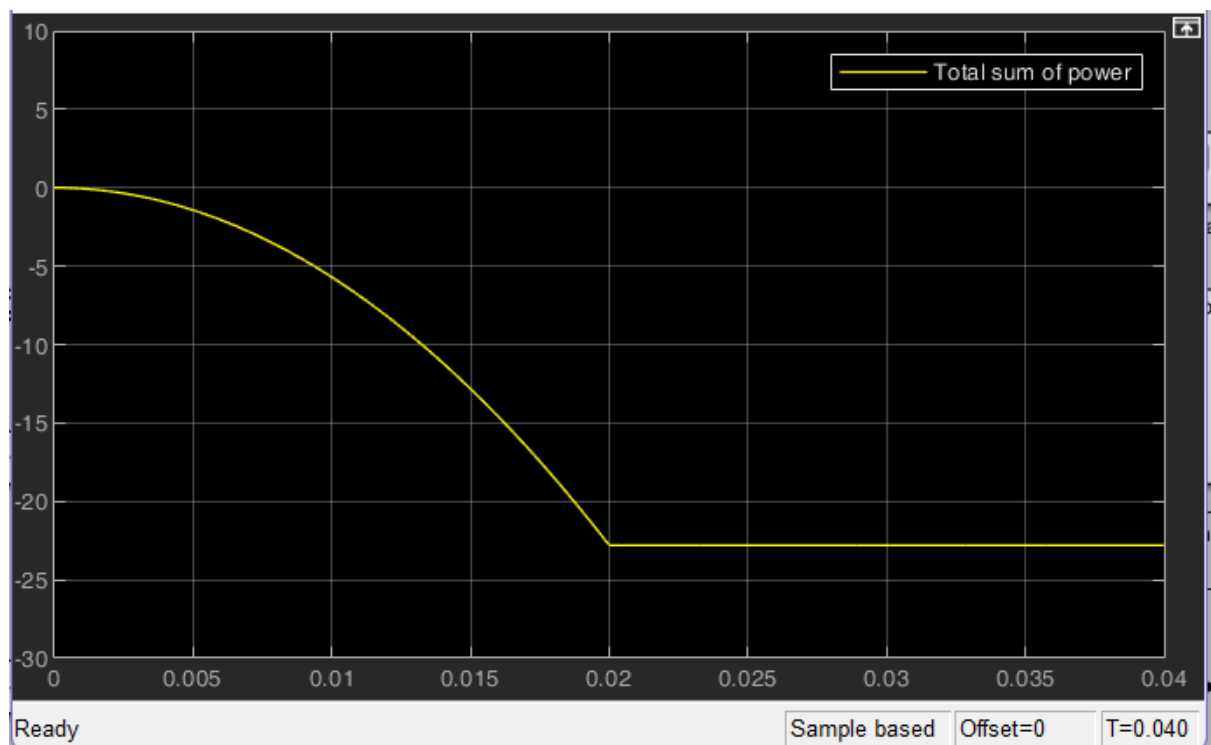

Result :

The total power in a three-phase power system is constant with respect to time(after steady state), which can be verified through this graph.

Scope 3 : V_line and V_phase Graph

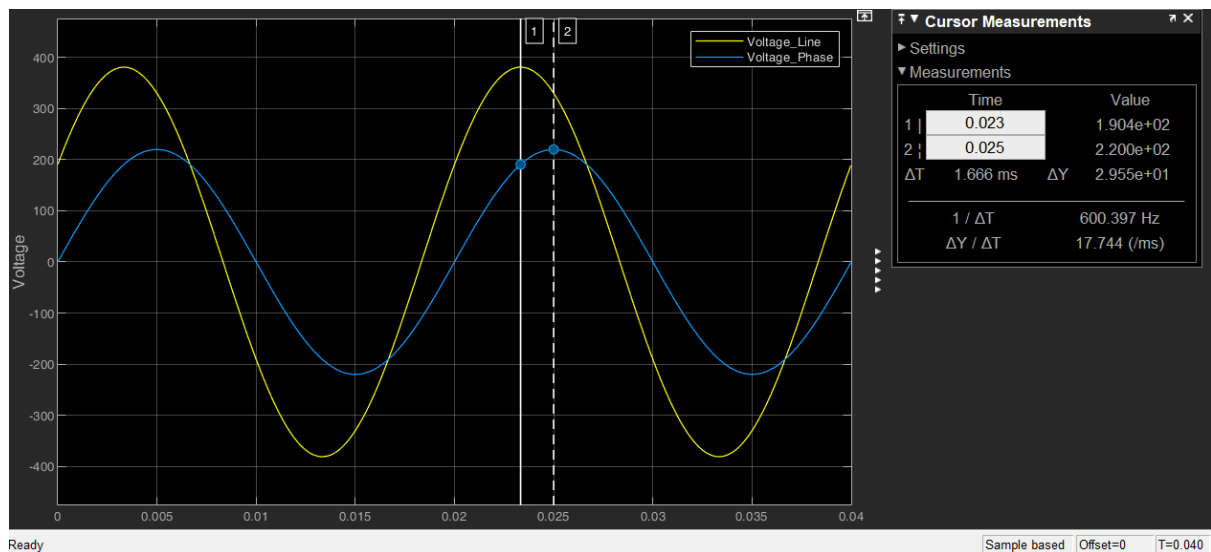

Result:

- ΔT between the peaks of V_{phase} and V_{line} comes out to be 1.666 ms As Phase Difference = $\omega \Delta t$

$$= 2\pi f \times \Delta t$$

$$= 2\pi f \times 1.666 \times 0.001 = 0.523$$

Which is in radians, when we convert it into degrees, it comes out to be 29.998 degrees which is approximately equal to 30 degrees.

Therefore, V_{phase} leads V_{line} by 30 degrees.

- Also through Display, $V_{\text{line}} = 269.4 \text{ V}$


$$V_{\text{phase}} = 155.6 \text{ V}$$

And their ratio comes out to be 1.732 .


- Reactive Power from 3 phase power measurement is -22.81 VAR, and from Single Phase Power reactive power is -7.603 VAR their ratio is 3. Same is the case with Real power.

For other values of R,L and C :

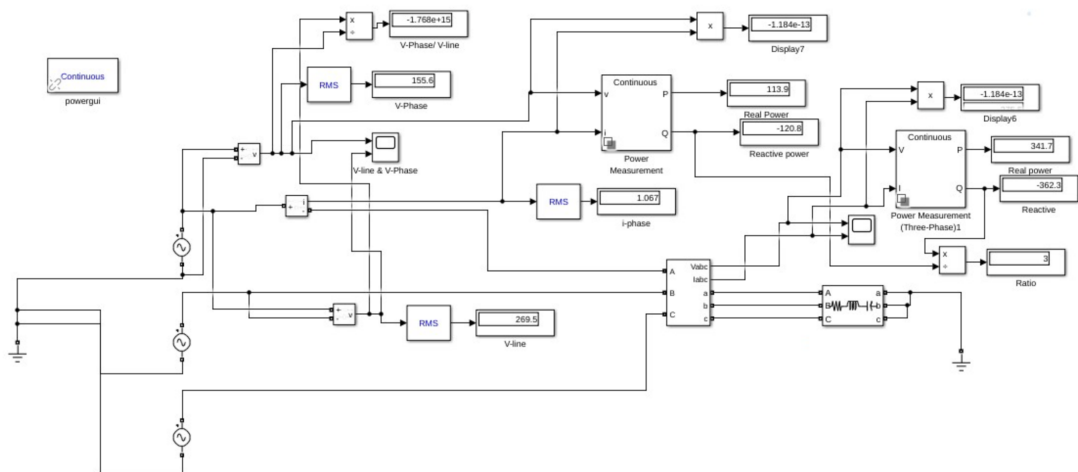For $R=100\ \Omega$, $L=10^{-4}\text{ H}$, $C=10^{-5}\text{ F}$



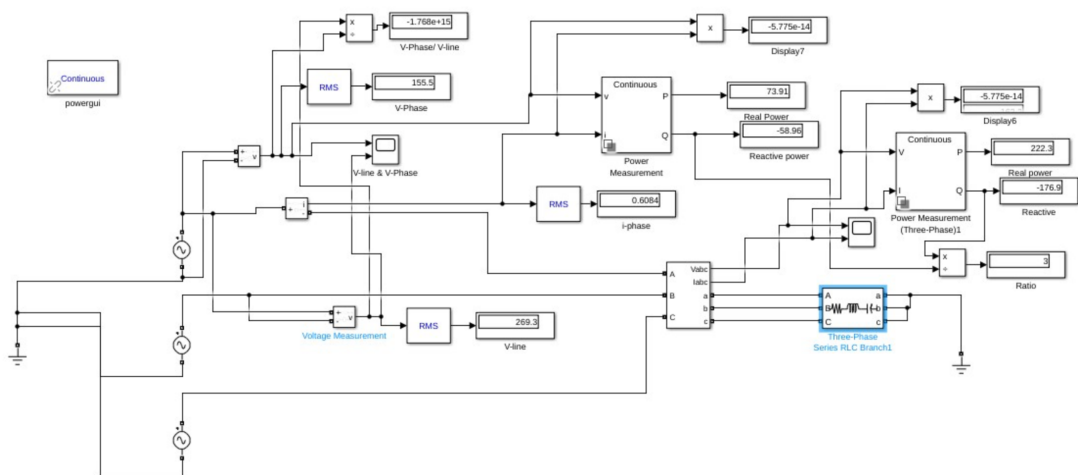For $R=200\ \Omega$, $L=2 \times 10^{-4}\text{ H}$, $C=2 \times 10^{-5}\text{ F}$



All the properties of Graphs and circuit remain the same, just value differs in these two cases.

Conclusions:

1. V_{line} is 3 times the V_{phase} voltage , $I_{\text{line}} = I_{\text{phase}}$.
2. 3-Phase Power is 3 times the Single phase power.
3. V_{line} leads V_{phase} by 30 Degrees.
4. Total power of the system is constant.
5. At any point the sum of current of phase A, B and C is equal to Zero, that's why current through the neutral line is zero.