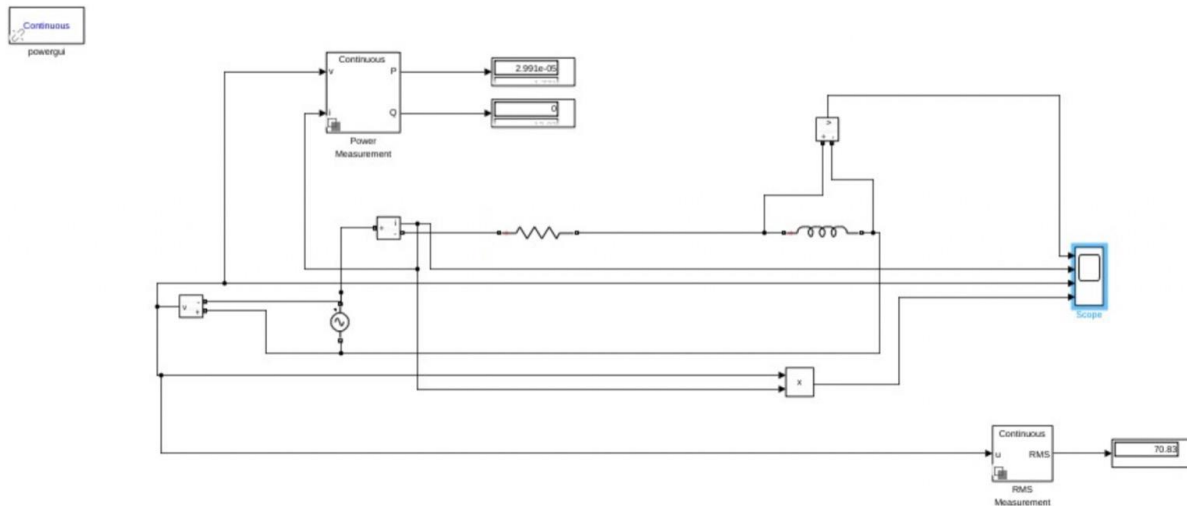


EE EXPERIMENT 2



NAME : Karan Acharya

Student ID.: 202251064


RL Circuit:



Scope output:

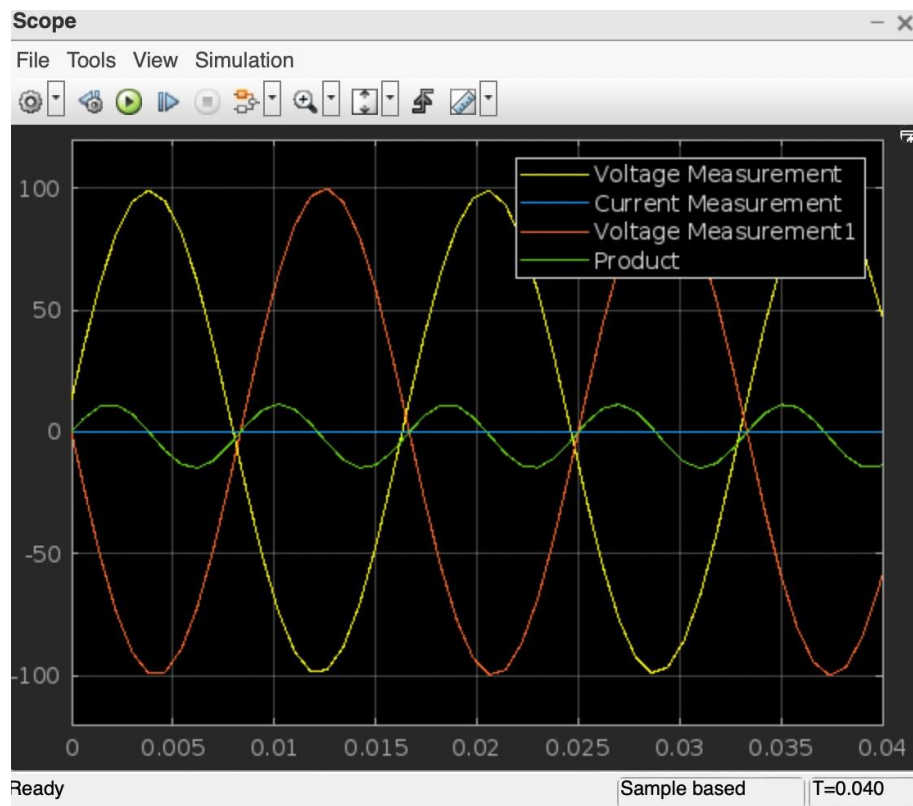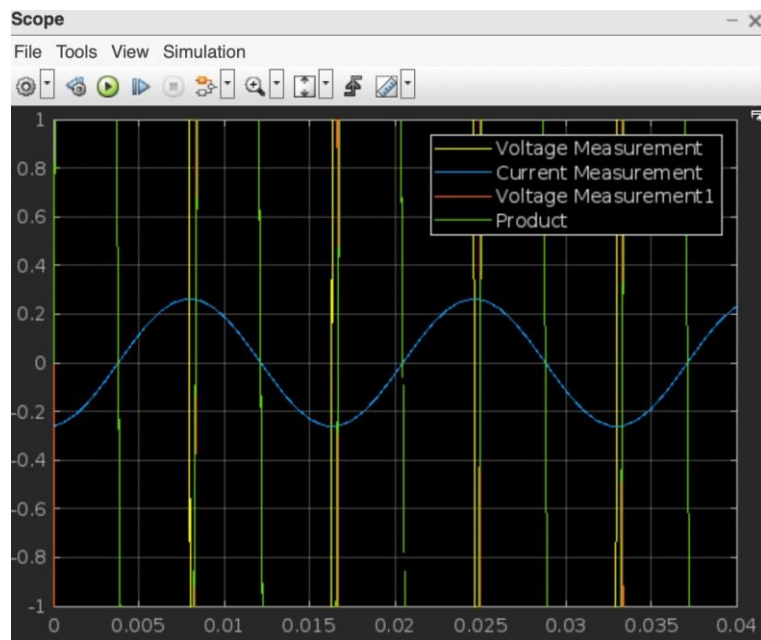

RC circuit:

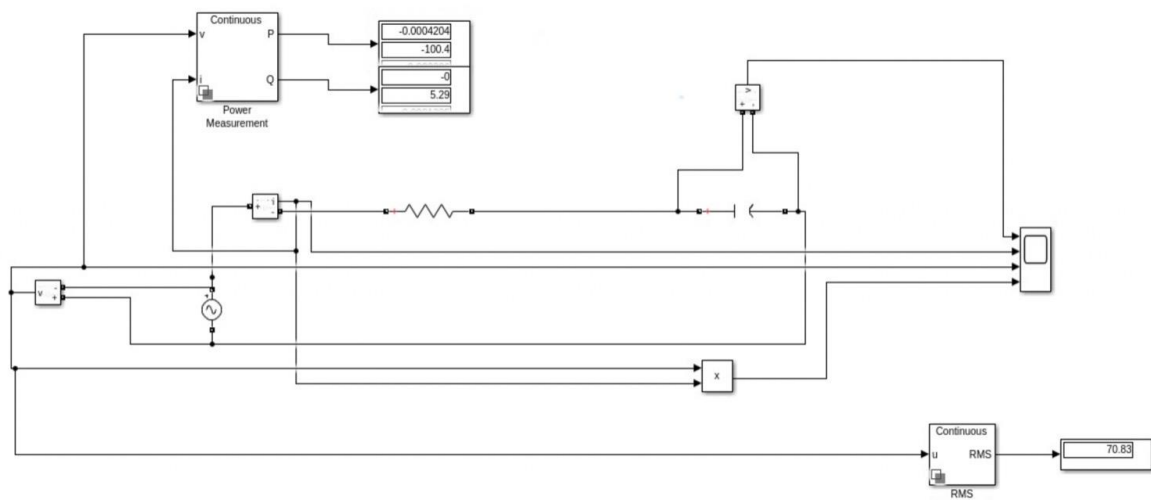

Scope Output:

